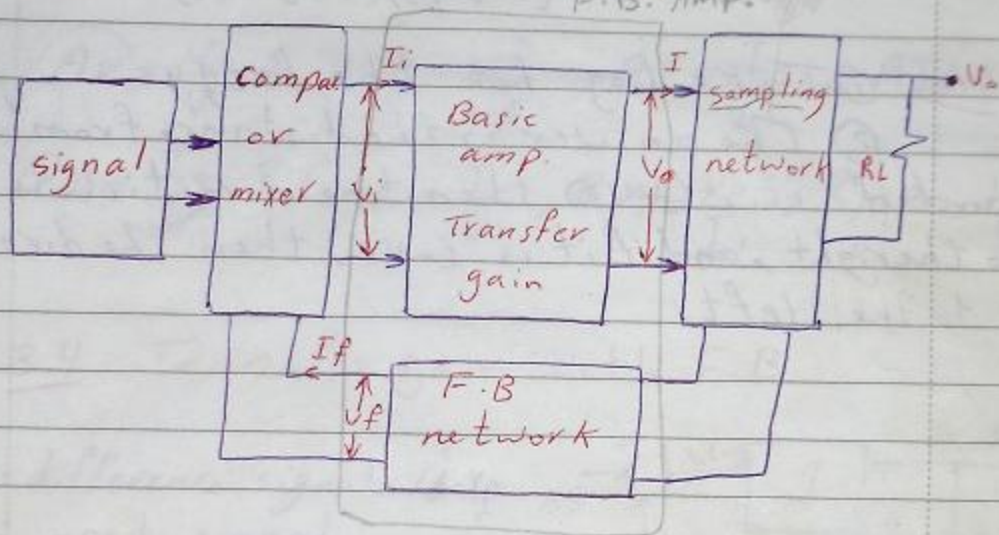



3.2 Feed Back Concept:

F.B. Amp.




3.2.1 Sampling network:

It is either voltage or current gain

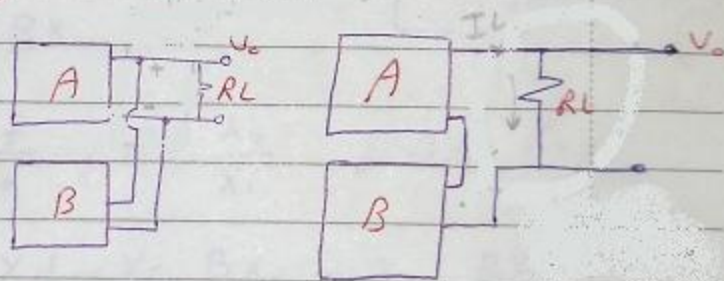

3.2.2 Comparator or Mixer

It is either series or shunt mixer

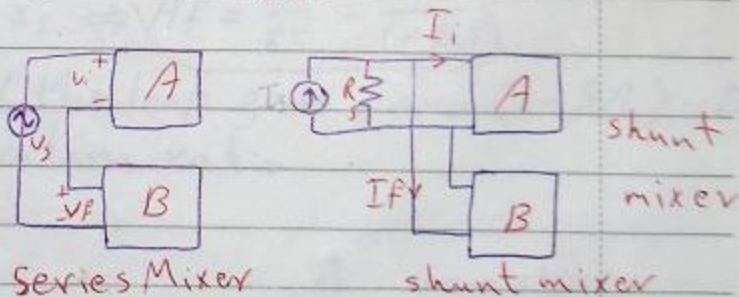

3.3 Transfer ratio or gain:

$$A_V = \frac{V_o}{V_i} \text{ \& } A_{Vf} = \frac{V_o}{V_s}, \quad A_I = \frac{I_o}{I_i} \text{ \& } A_{If} = \frac{I_o}{I_s}$$

$$G_M = \frac{I_o}{V_i} \text{ \& } G_{Mf} = \frac{I_o}{V_s}, \quad R_M = \frac{V_o}{I_i}, \quad R_{Mf} = \frac{V_o}{I_s}$$


3.4 Transfer gain with F.B.

x_d = difference signal = $x_s - x_f$

x_s = input signal.

x_o = o/p signal = Ax_i

x_f = F.B signal = Bx_o

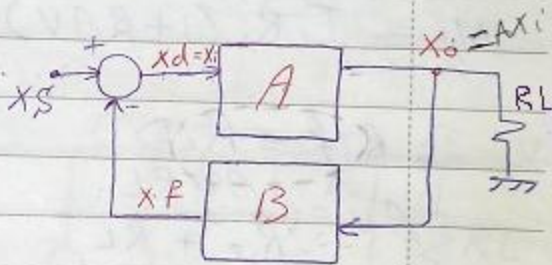

We have $\beta = \frac{x_f}{x_o}$, $A = \frac{x_o}{x_i}$, $Af = x_o/x_s$

$$x_i = x_s - x_f = x_d = x_s - \beta x_o = x_s - \beta A x_i$$

$$\therefore (1 + \beta A) x_i = x_s \Rightarrow Af = \frac{x_o}{x_s} = \frac{A}{1 + \beta A}$$

βA is called the loop gain, and $(1 + \beta A) = D$ is called the return ratio

3.5.1 Input Resistance of voltage series

$$R_i = R_i' + R_s, \beta = V_f / V_o$$

$$V_s = V_i + V_f$$

$$= V_i + \beta V_o$$

$$= V_i + \beta A V_i$$

$$= V_i (1 + \beta A V)$$

$$V_i = I_i R_i$$

$$V_s = I_i R_i (1 + \beta A V) \quad \therefore \frac{V_s}{I_i} = R_{if} = R_i (1 + \beta A V)$$

$$\therefore R_{if} = R_i D$$

$$A V = \frac{A V R_L}{R_o + R_L}$$

$$\text{or } A V = \lim_{R_L \rightarrow \infty} A V$$

3.5.2 Input Resistance of current shunt F.B.



Similarly

$$\beta = I_f / I_o, R_{if} = \frac{R_i}{D}$$

$$D = (1 + \beta A I)$$

$$A I = \frac{A_i R_o}{R_o + R_L}$$
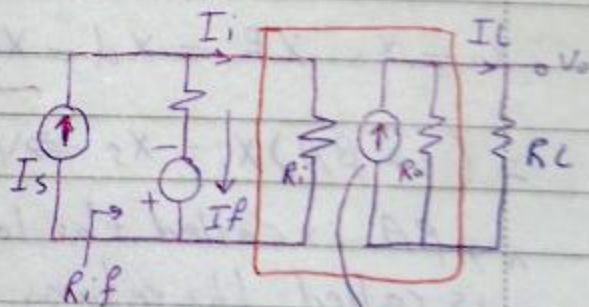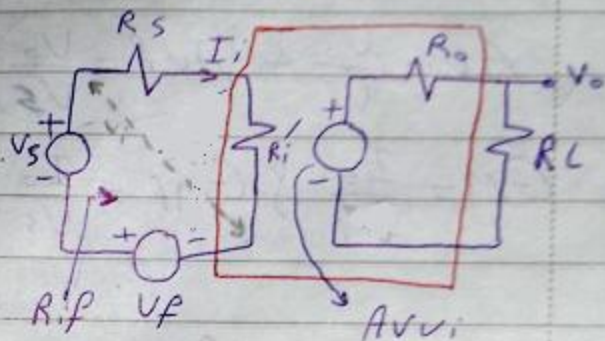
$$A_i = \lim_{R_L \rightarrow \infty} A I$$



$$R_i = R_i' \parallel R_s$$


3.5.3 Input Resistance of current series F.B.

$$\beta = V_f / I_o$$

$$R_{if} = R_i D, D = (1 + \beta G_m)$$

$$G_m = \lim_{R_L \rightarrow \infty} G_m$$

$$G_m = G_m R_o / (R_o + R_L)$$

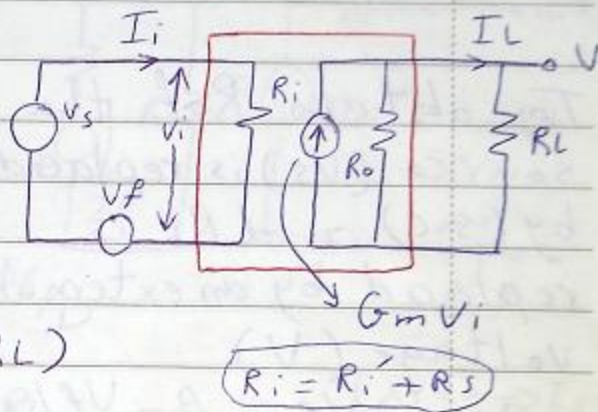

3.5.4 Input Res. of voltage shunt.

$$\beta = I_f / V_o, D = (1 + \beta R_m)$$

$$R_{if} = R_i / D$$

$$R_m = R_m R_L / (R_o + R_L)$$

$$R_m = \lim_{R_L \rightarrow \infty} R_m$$

