


Ex. For the ckt shown, The transistors are identical and having the following parameters $h_{ie} = 1K\Omega$, $h_{fe} = 50$, $h_{re} = h_{oe} = 0$. $C_b = 0.1\mu F$, $C_z = 4.7\mu F$

(a) Find $\frac{A_{VS}}{A_{VS0}}$

(b) Estimate the lower 3dB freq

Ans.

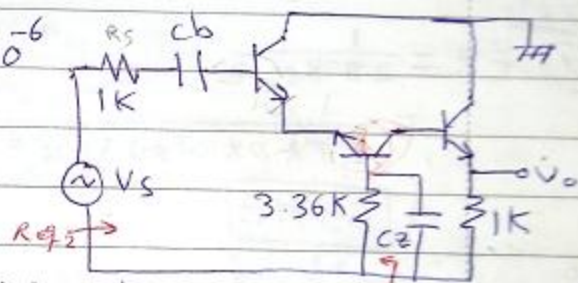(a) $f_z = \frac{1}{2\pi \times 3.36 \times 10^3 \times 4.7 \times 10^{-6}}$
 $= 10 \text{ Hz}$



$f_{P1} = \frac{1}{2\pi [3.36K \parallel (h_{ie} + h_{ie} + 1K)] \times 4.7 \times 10^{-6}}$
 $= 21.36 \text{ Hz}$

$f_{P2} = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times (1K + h_{ie} + h_{ie})} = 530.5 \text{ Hz}$

$\alpha = f_{P1} / f_z = 2.1$

$\therefore \frac{A_{VS}}{A_{VS0}} = \frac{1}{2.1} \frac{(1 + j f / 10)}{(1 + j f / 21.3)(1 - j 530.5 / f)}$


(b) Since $f_{P2} \gg$ from the others by more than 2 octaves then $f_L = f_{P2}$.

$0.707 = \frac{1}{\sqrt{(1 + f^2 / 13^2)(1 + 5^2 / f^2)}}$


$\left| \frac{A_{VS}}{A_{VS0}} \right| = \frac{10(1 + f / 13)}{(1 + f / 13)(1 - j 5 / f)}$

2.6 High freqy response of two stage CE transistor:


$$r_{bb'} = 100\Omega$$

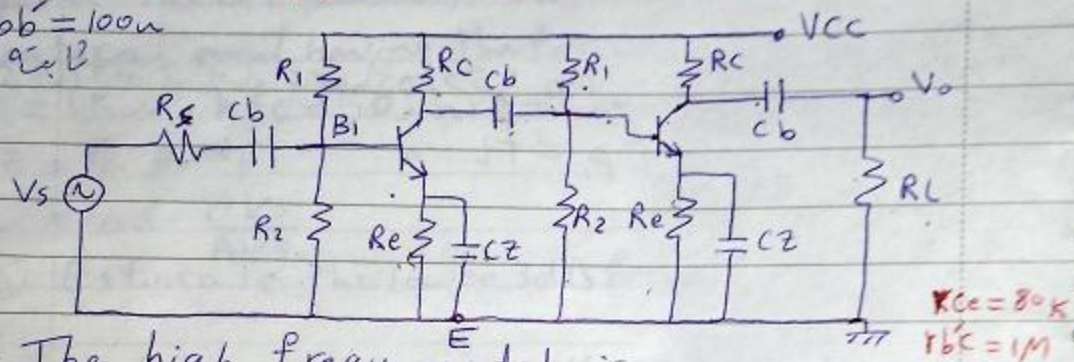

* The high freqy model is:

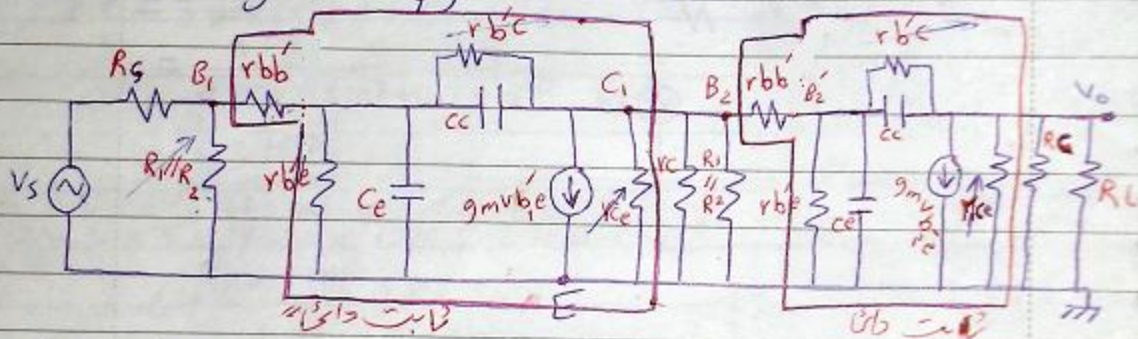

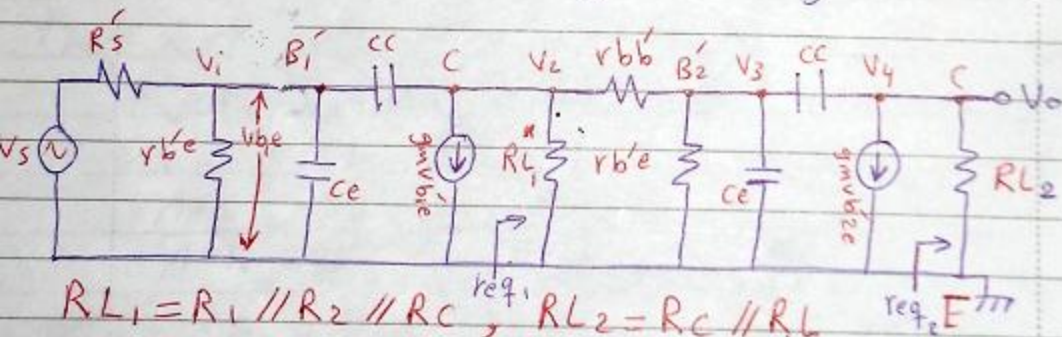* Usually $R_L \ll 2K\Omega$, and since $R_{b'c}$, r_{ce} are very large compared with R_L so they can be Neglected. Take $R_1 \parallel R_2 \gg R_i$ so they can be neglected too.



$$R_{L1} = R_1 \parallel R_2 \parallel R_C, \quad R_{L2} = R_C \parallel R_L$$

$$R_s' = R_s + r_{bb'}, \quad V_{b'e} = V_1, \quad V_{b'c} = V_2$$

$$V_4 = V_o, \quad V_o?$$

(18)

$$r_{eq1} = R_{L1} \parallel (r_{bb'} + r_{b'e})$$

$$r_{eq2} = R_{L2}$$

$$(V_1 - V_5) / R_s + V_1 (1/r_{b'e} + 1/x_{ce}) + (V_1 - V_2) / x_{cc} = 0 \quad \text{--- ①}$$

$$(V_2 - V_1) / x_{cc} + g_m V_1 + V_2 / R_{L1} + (V_2 - V_3) / r_{b'b'} = 0 \quad \text{--- ②}$$

$$(V_3 - V_2) / r_{b'b'} + V_3 (1/r_{b'e} + 1/x_{ce}) + (V_3 - V_4) / x_{cc} = 0 \quad \text{--- ③}$$


$$(V_4 - V_3) / x_{cc} + g_m V_3 + V_4 / R_{L2} = 0 \quad \text{--- ④}$$

Solving and find V_o ?

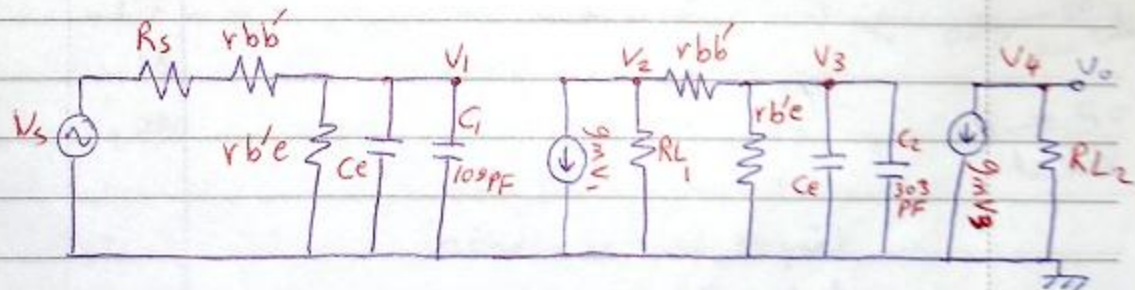2.7 Two stage Cascade Simplify Analysis:

It is approximated by using Miller's theorem, C_c of Q_2 is replaced by $C_c(1 + g_m R_{L2})$ and C_c of Q_1 are replaced by $C_c(1 + g_m \times R_{L1} // (r_{b'e} + r_{b'b'}))$

Since $C_e = 100\text{PF}$, $C_c = 3\text{pF}$, $r_{b'e} = 1\text{K}\Omega$, $r_{b'b'} = 100\Omega$, $g_m = 50\text{ mA/V}$, $R_s = 50\Omega$, So new C_c of $Q_2 = 3 \times (1 + 50 \times 2) = 303\text{pF}$, and new C_c of $Q_1 = 109\text{PF}$, & the cct. will be:



Ex. Sketch Magnitude & phase for



$$\frac{A_{VS}}{A_{VS_0}} = \frac{1}{16} \frac{(1+jf/0.5)}{(1+jf/3)(1+jf/50)}$$

$$20 \log \frac{1}{16} = -24 \text{ dB}$$

$\left| \frac{A_{VS}}{A_{VS_0}} \right| \text{ dB}$

$\leftarrow - \quad + \rightarrow$

0.5 1 2 30
205 1 25 10 27.1

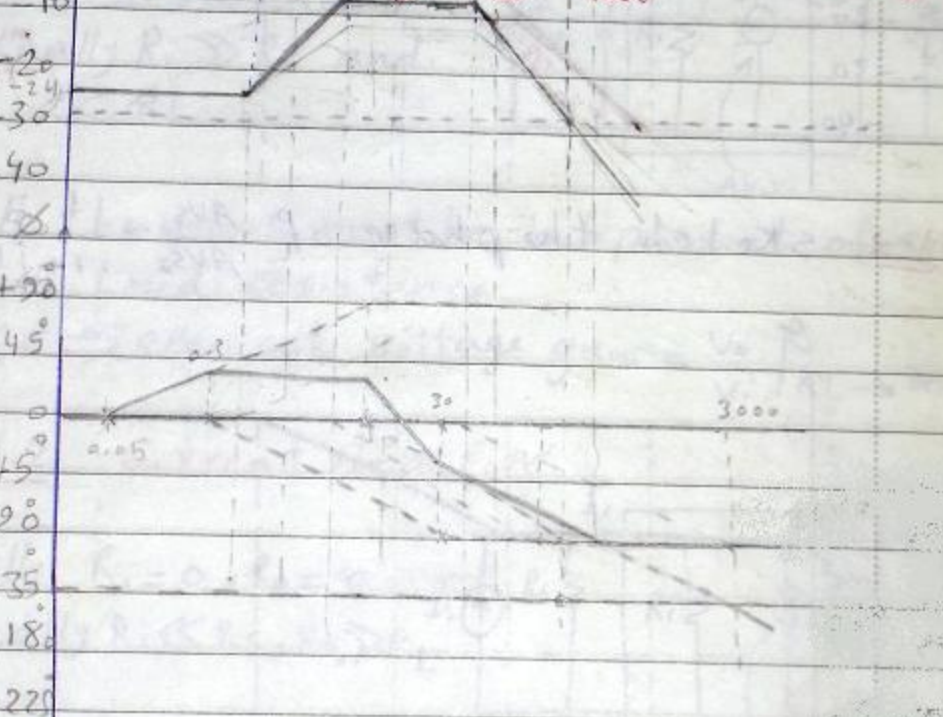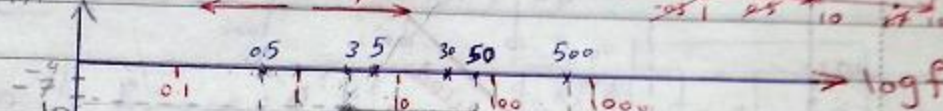


الموضوع

Ex. Sketch Magnitude & phase for


$$\frac{A_{Vs}}{A_{Vs_0}} = \frac{1}{16} \frac{(1+jf/0.5)}{(1+jf/3)(1+jf/50)}$$
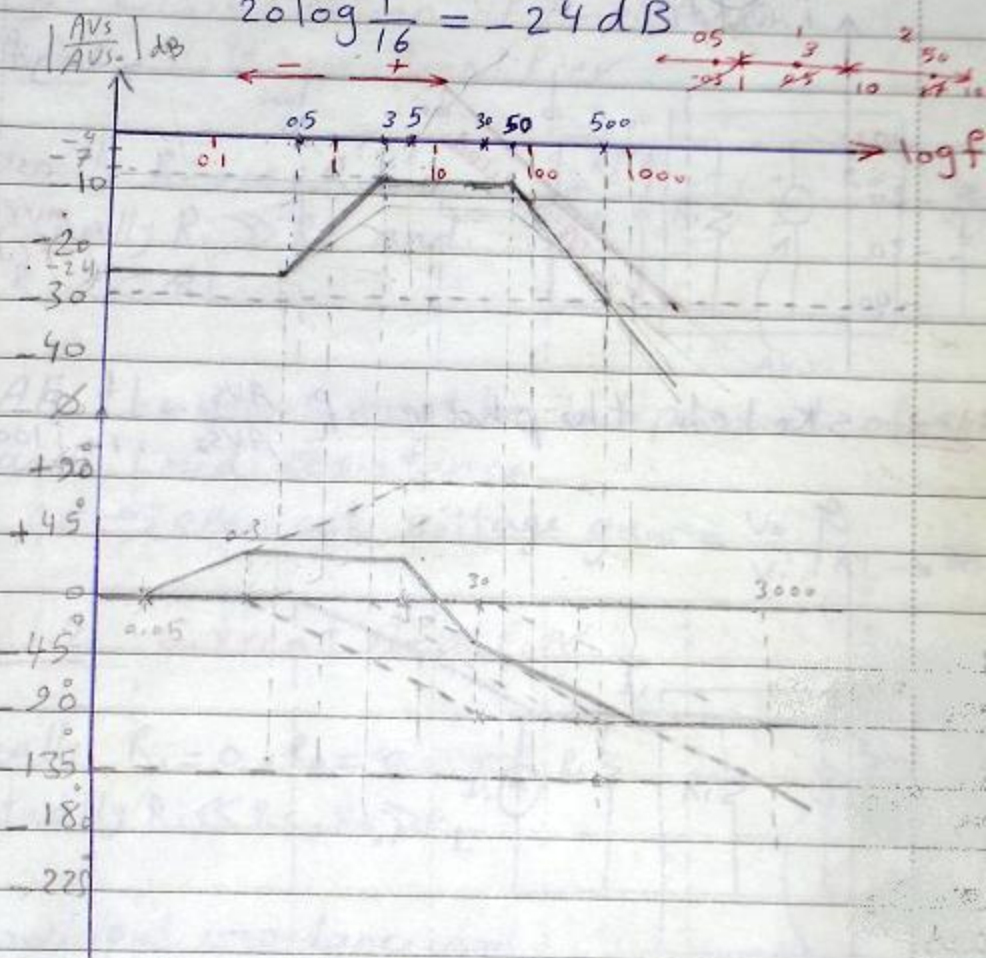
$$20 \log \frac{1}{16} = -24 \text{ dB}$$



Ex. Sketch the Magnitude of:
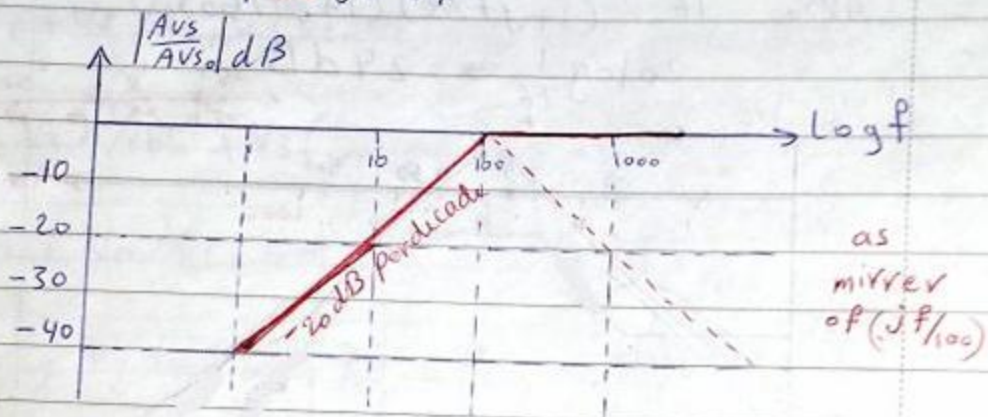
$$\frac{A_{Vs}}{A_{Vs_0}} = \frac{1}{1-j100/f}$$



H.W sketch the phase of $\frac{A_{Vs}}{A_{Vs_0}} = \frac{1}{1-j100/f}$

$$(V_1 - V_s) \left(\frac{1}{R_s + r_{bb'}} \right) + V_1 \left[\frac{1}{r_{be}} + \frac{1}{x_{ce}} + \frac{1}{x_{c1}} \right] = 0 \quad \text{--- (1)}$$

$$g_m V_1 + V_2 \frac{1}{R_{L1}} + (V_2 - V_3) \frac{1}{r_{bb'}} = 0 \quad \text{--- (2)}$$

$$(V_3 - V_2) \frac{1}{r_{bb'}} + V_3 \left(\frac{1}{r_{be}} + \frac{1}{x_{ce}} + \frac{1}{x_{c2}} \right) = 0 \quad \text{--- (3)}$$

$$g_m V_3 + V_0 \frac{1}{R_{L2}} = 0 \quad \text{--- (4)}$$

Solving by taking $R_{L1} = R_{L2} = 2 \text{ k}\Omega$

$$A_{VS} = \frac{V_o}{V_s} = \frac{2810}{(1 + jf/5.85 \times 10^5)(1 + jf/5.85 \times 10^6)} \quad \text{H.w.}$$

The cct. has two poles, $f_1 = 0.585 \text{ MHz}$
and $f_2 = 5.85 \text{ MHz}$, $f_H = f_1$

H.w. For the cct shown, The transistors are identical and having the following parameters.
 $h_{ie} = 1 \text{ k}\Omega$, $h_{fe} = 50$, $h_{re} = h_{oe} = 0$, $C_b = 0.1 \text{ }\mu\text{F}$,
 $C_z = 0.3 \text{ }\mu\text{F}$

(a) Find A_{VS}

(b) Estimate the lower 3dB freq

