

CHAPTER 3

Feed Back Amplifiers


3.1 Classification of Amplifiers

3.1.1 Voltage Amplifier

Ideally $R_i = \infty, R_o = 0$

Actually $R_i \gg R_s$ and:

$R_o \ll R_L$.

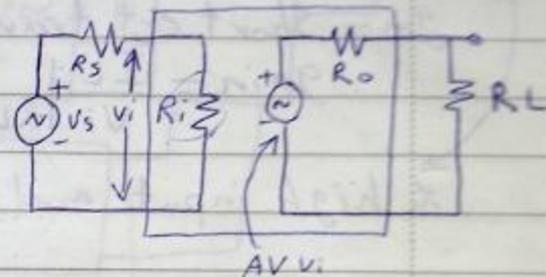


* All the gains must be independent of source and Load resistance.

$AV \Rightarrow$ open cct. voltage gain = $\frac{V_o}{v_i} | R_L \rightarrow \infty$

3.1.2 Current Amplifier.

Ideally $R_i = 0, R_o = \infty$

Actually $R_i \ll R_s, R_o \gg R_L$

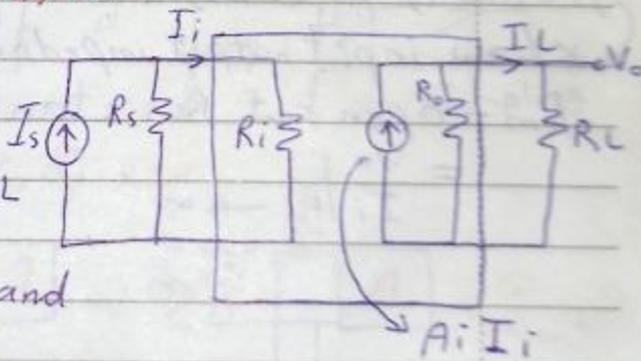


* Low input impedance and high output impedance

$A_i =$ short cct. current gain

$= I_L / I_i | R_L \rightarrow \infty$

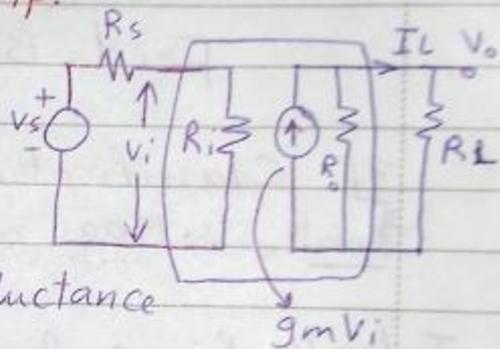3.1.3 Trans. conductance Amp.

Ideally $R_i = \infty, R_o = \infty$
Actually $R_i \gg R_s, R_o \gg R_L$



$g_m =$ short ckt trans conductance


$$\text{gain} = \frac{I_L}{V_i} \Big|_{R_L \rightarrow 0}$$

* high input and output impedances

3.1.4 Transistance Amp.

Ideally $R_i = 0, R_o = 0$

Actually $R_i \ll R_s, R_o \ll R_L$

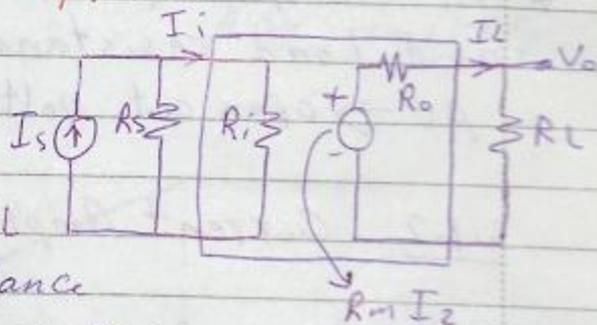

* Low input output impedance

$R_m =$ open ckt Resistance gain

$$= \frac{V_o}{I_i} \Big|_{R_L \rightarrow \infty}$$