

Subtractors

Subtraction is the other basic function of arithmetic operations of information-processing tasks of digital computers. Similar to the addition function, subtraction of two binary digits consists of four possible elementary operations, which are $0-0 = 0$, $0-1 = 1$ with borrow of 1, $1-0 = 1$, and $1-1 = 0$. The first, third, and fourth operations produce a subtraction of one digit, but the **second operation produces a difference bit as well as a borrow bit**. The borrow bit is used for subtraction of the next higher significant bit. A **combinational circuit** that performs the subtraction of two bits as described above is called a half-subtractor. The digit from which another digit is subtracted is called the minuend and the digit which is to be subtracted is called the subtrahend.

When the minuend and subtrahend numbers contain more significant digits, the borrow obtained from the subtraction of two bits is subtracted from the next higher-order pair of significant bits. Here the **subtraction operation involves three bits**—the **minuend bit**, **subtrahend bit**, and the **borrow bit**, and produces a different result as well as a borrow. The combinational circuit that performs this type of addition operation is called a full-subtractor. Similar to an adder circuit, a full-subtractor combinational circuit can be developed by using two half-subtractors.

Design of Half-subtractors

A half-subtractor has **two inputs** and **two outputs**. Let the input variables minuend and subtrahend be designated as **X** and **Y** respectively, and output functions be designated as **D** for **difference** and **B** for **borrow**. The truth table of the functions is as follows.

<i>Input variables</i>		<i>Output variables</i>	
<i>X</i>	<i>Y</i>	<i>D</i>	<i>B</i>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

By considering the minterms of the truth table, the Boolean expressions of the outputs D and B functions can be written as:

$$D = X'Y + XY' \quad \text{and} \quad B = X'Y.$$

Figure 1 shows the logic diagram to realize the half-subtractor circuit.

 


Figure (1)

Design of Full-subtractors

A combinational circuit of full-subtractor performs the operation of subtraction of **three bits**—the minuend, subtrahend, and borrow generated from the subtraction operation of previous significant digits and produces the outputs difference and borrow. Let us designate the input variables minuend as X, subtrahend as Y, and previous borrow as Z, and outputs difference as D and borrow as B. Eight different input combinations are possible for three input variables. The truth table is shown below according to its functions.

Input variables			Outputs	
X	Y	Z	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

	Y'Z'	Y'Z	YZ	YZ'
X'		1		1
X	1		1	

Figure 2(a) Map for function D.

	Y'Z'	Y'Z	YZ	YZ'
X'		1	1	1
X			1	

Figure 2(b) Map for function B.

Karnaugh maps are prepared to derive simplified Boolean expressions of D and B as in Figures 2(a) and 2(b), respectively.

The simplified Boolean expressions of the outputs are:

$$D = X'Y'Z + X'YZ' + XY'Z' + XYZ \text{ and}$$

$$B = X'Z + X'Y + YZ.$$

The logic diagram for the above functions is shown in Figure 3.

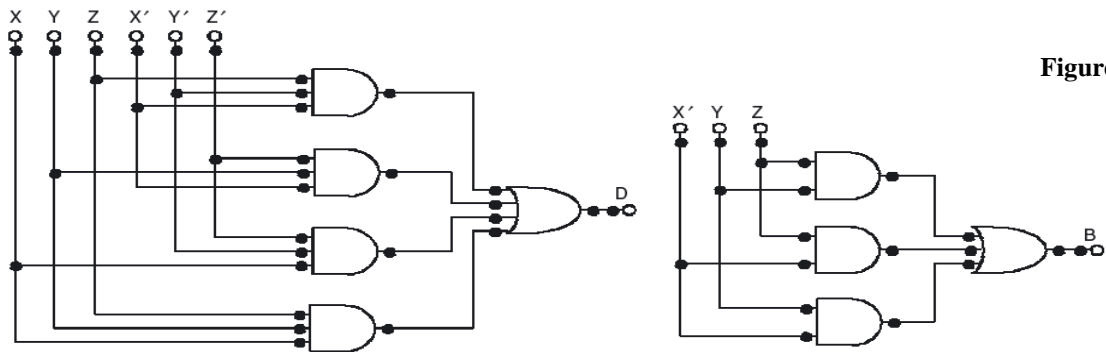


Figure 3

Similar to a full-adder circuit, it should be noticed that the configuration of the combinational circuit diagram for full-subtractor as shown in Figure 3 contains two-input and three-input AND gates, and three-input and four-input OR gates. Other configurations can also be developed where number and type of gates are reduced. For this, the Boolean expressions of D and B are modified as follows.

$$D = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

$$= X' (Y'Z + YZ') + X (Y'Z' + YZ)$$

$$= X' (Y \oplus Z) + X (Y \oplus Z)'$$

$$= X \oplus Y \oplus Z$$

$$B = X'Z + X'Y + YZ = X'Y + Z(X' + Y)$$

$$= X'Y + Z(X'Y + X'Y' + XY + X'Y)$$

$$= X'Y + Z(X'Y + X'Y' + XY)$$

$$= X'Y + X'YZ + Z(X'Y' + XY)$$

$$= X'Y + Z(X \oplus Y)'$$

Logic diagram according to the modified expression is shown in Figure 4.

 


Figure 4

Note that the full-subtractor developed in Figure 4 consists of two 2-input AND gates, two 2-input XOR (Exclusive-OR) gates, two INVERTER gates, and one 2-input OR gate. This contains a reduced number of gates as well as type of gates as compared to Figure 3. Also, it may be observed, if compared with a half-subtractor circuit, the full-subtractor circuit can be developed with two half-subtractors and one OR gate.