



Digital Electronic

Dr. Ehssan Al-Bermamy
Assist. Prof.

2nd semester
2018-2019



© Dr. E. Al-Bermamy, Department of Physics, University of Babylon, 2019.



Chapter Two

Lecture 4

2

© Department of Physics, University of Babylon, 2019.

Logic Gates

- This chapter is devoted to **practically apply the concept of binary digits to circuits.**
- Logic gates are “**elementary bricks**” used in the construction of **digital circuits.**
- A logic gate is **a special type of circuit designed to accept (inputs) and generate (outputs) voltages signals corresponding to binary digits (1 and 0).**

© Department of Physics, University of Babylon, 2019.

Digital signals and gates:

- Let us consider the following circuit:
- When the **switch** is **connected to the ground (0V)**, the light emitting diode (LED) does **not** shine.
- If we were using **this circuit to represent binary digits**, that means **the input signal is a binary “0”** and the **output is a binary “0”** or that the output is at **the low logic level.**
- Moving the switch to the other **position (Vcc)**, Means **a binary “1” is the input and receive a binary “1” at the output.** The **output** is also said to be at **the high logic level.**

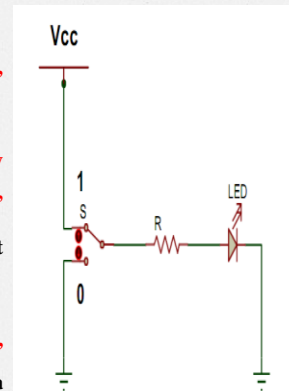


Figure 2.1: Logic circuit.

© Department of Physics, University of Babylon, 2019.

Digital signals and gates:

- This gate shown by this **simple circuit** is a “buffer” or “yes” gate, because **the logic state of its input is identical to that of its output.**
- Many types of gates are used in **digital electronics**: **single** input gates like the **buffer** and the **NOT** gates; **multiple** inputs gates like **AND, NAND, OR, NOR** and **XOR** gates.
- The **aim** of this chapter is to **study the functioning of each of those logic gates** and also how they can be **combined to design a simple logic function.**

© Department of Physics, University of Babylon, 2019.

5

➤2.3 The NOT gate:

- The **NOT gate or Inverter** is a logic gate which functions in such a way that the logic state of the **output** is exactly the **opposite** of that of the **input.**
- **Remark 2.1: The truth table**
A truth table is a **standard way of representing the Inputs/outputs relationships of a digital circuit**, listing all the possible input logic level combinations with their respective output logic levels.
- The NOT gate truth table:

© Department of Physics, University of Babylon, 2019.

6

The NOT gate truth table:

- The NOT gate truth table:

Input	Output
0	1
1	0

- Symbol



© Department of Physics, University of Babylon, 2019.

7

Remark 2.2: the buffer gate

- If two inverter gates were connected together, the output of one fed into the input of another.
- The two inversion functions would “cancel” each other out so that there would be no inversion from input to final output.



Figure 2.2: Principle of the buffer gate

- A buffer is a special logic gate manufactured to perform the same function as two inverters connected together.
- Buffer gates serve to amplify signals, taking a weak signal source that is not capable of providing much current, and boosting the current capacity of the signal so as to be able to drive a load.

© Department of Physics, University of Babylon, 2019.

8

- Symbol of a buffer gate:



- Truth table of the buffer gate:

Input	Output
0	0
1	1

© Department of Physics, University of Babylon, 2019.

2.4 Multiple input gates:

- With a **single input** gate such as the **inverter or buffer**, there can **only be two possible input states**: either 1 or 0.
- With **multiple input** gates, **many** possibilities are available for input states.
- The number of possible input states is **equal to two to the power of the number of inputs**. So, if a gate has **n inputs**, therefore there are **2^n** possible input combinations.

© Department of Physics, University of Babylon, 2019.

10

2.4.1 The AND gate:

- The output of the AND gate is **high** if and only if **all inputs are high**.
- If any input is **low**, the **output** is **guaranteed** to be in a **low** state as well.
- **Truth table:**
- Let us draw the truth table of a two inputs AND gate

© Department of Physics, University of Babylon, 2019.

//

2.4.1 The AND gate Truth table:

- Let us draw the truth table of a **two inputs AND** gate

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

- The **output** is **high** only when **all the two inputs** are **high**.

- **Symbol**



© Department of Physics, University of Babylon, 2019.

//


Exercises

Exercise 2.1:

Draw the truth table of a three inputs AND gate.

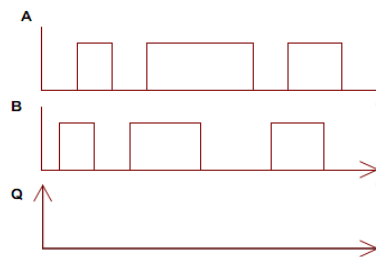Exercise 2.2:

Complete the chronogram of the output Q of a two inputs AND gate.



© Department of Physics, University of Babylon, 2019.

13


Exercises

Exercise 2.1:

Draw the truth table of a three inputs AND gate.

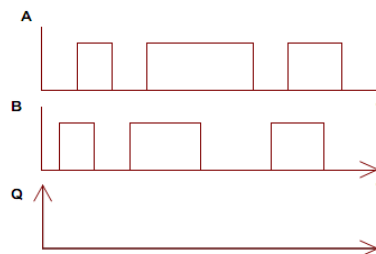Exercise 2.2:

Complete the chronogram of the output Q of a two inputs AND gate.



© Department of Physics, University of Babylon, 2019.

14

Changing of base:

We have already seen in the previous section **how to change from binary to decimal, octal or hexadecimal systems of numeration**. The present section is intended to show how to move from a given system of numeration to any other system.

From octal and hexadecimal to binary and decimal:

- The **octal and hexadecimal** systems are actually used by **computer engineer** just to obtain a “shorthand” representation of **binary numbers** (because octal and hexadecimal representations take a **few numbers of ciphers or symbols as compared to binary system**).
- Only **binary system** is implemented in the **electronic circuits of digital systems** (through two levels of **voltages or currents**: high (1) and low (0)), the others systems being used by engineers just for simplification issues.
- However, we sometimes have the **need to convert either of those systems to binary or decimal forms**.

© Department of Physics, University of Babylon, 2019.

2.4.3 The OR gate:

- The **output** of the **OR** gate is **high** if **any** of the **inputs** is **high**.
- The **output** of an OR gate goes **low** if and only if all inputs are low.

• Truth table:

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

• Symbol:



© Department of Physics, University of Babylon, 2019.


16

Exercise 2.4:

Draw the truth table of a three inputs OR gate.

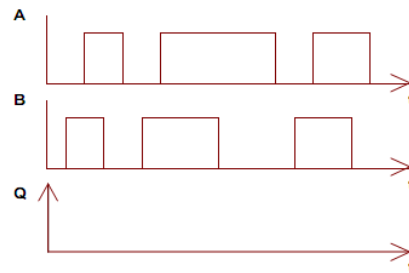Exercise 2.5:

Complete the chronogram of the output Q of a two inputs OR gate.




© Department of Physics, University of Babylon, 2019.

17

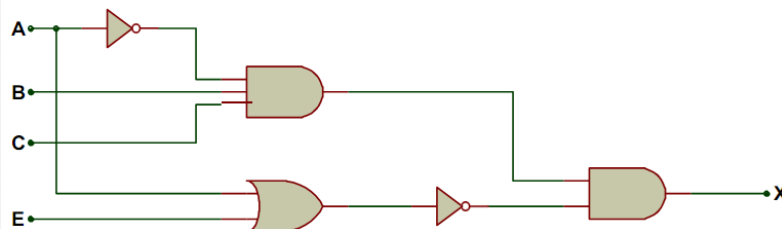Exercise 2.6:

Let us consider the following digital circuit:



- Give the expression of the output X.
- Draw the truth table of the digital circuit.

© Department of Physics, University of Babylon, 2019.

18


Exercise 2.7:

Draw the truth table of the digital circuit described by the following equation:

$$X = AB + A\overline{B}C + A\overline{C}$$

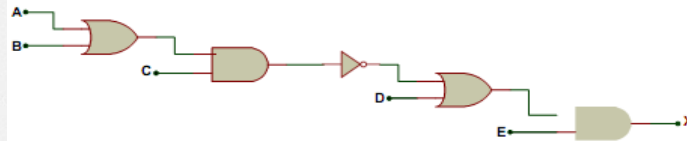Exercise 2.8:

Let us consider the following digital circuit:



- Give the expression of the output X.
- Draw the truth table of the circuit.
- Answer the two previous questions considering the following digital circuit:

