



Digital Electronic

Dr. Ehssan Al-Bermamy
Assist. Prof.

2nd semester
2018-2019



© Dr. E. Al-Bermamy, Department of Physics, University of Babylon, 2019.



Chapter Two

Lecture 5

2

© Department of Physics, University of Babylon, 2019.


2.4.4 The **NOR** gate:

- The **NOR** gate is an **OR** gate with its **output inverted**.

- Truth table:

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

- Symbol:

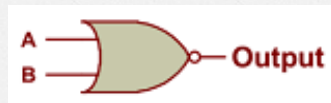


- The **NOR** gate can also be manufactured with more than **two inputs**.

© Department of Physics, University of Babylon, 2019.

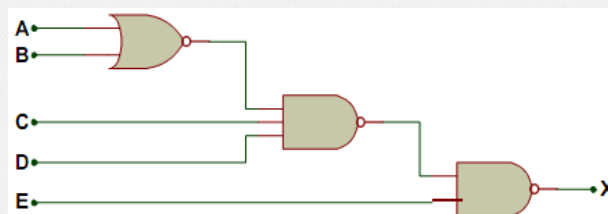Exercise 2.9:

- Let us consider the following digital circuit:




- a. Give the expression of the output X.
- b. Draw the truth table of the circuit.

© Department of Physics, University of Babylon, 2019.

Remark 2.3:

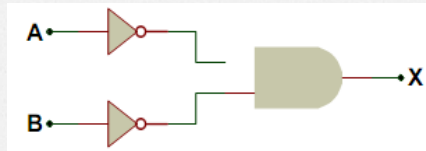- The negative **AND** gate and the negative **OR** gate.
- Let us consider the following digital circuit:



- a. Draw the truth table of this circuit.
- b. Show that this circuit is equivalent to a NOR gate.

© Department of Physics, University of Babylon, 2019.

5

Digital signals and gates:

- The **expression** of the **output X** can be written as follow: $X = \bar{A} \cdot \bar{B}$.
- Therefore, the **truth table** of the circuit can be easily deduced:

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

- We can notice that the **truth table** of this circuit is **identical** to that of a **NOR gate**.
- The gate described in this exercise is **called** the **negative AND gate** and its **symbol** is given as follow:




© Department of Physics, University of Babylon, 2019.

6

➤ Let us consider the following gate circuit:

➤ **Draw** the truth table of the circuit.

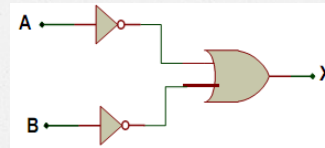➤ Show that the circuit is **equivalent to a NAND gate**.



➤ The **expression** of the **output X** can be written as follow: $X = \bar{A} + \bar{B}$.

➤ Therefore, the **truth table** of the circuit can be easily deduced:

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

© Department of Physics, University of Babylon, 2019.


7

➤ We can notice that the **truth table** of this circuit is identical to that of a **NAND gate**.

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

➤ The circuit described in this exercise is called **the negative OR gate**.

➤ Its **symbol** is given as follow:

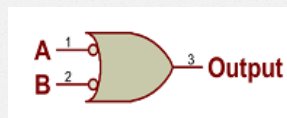

© Department of Physics, University of Babylon, 2019.

8

- The **previous remark** leads us to **two important theorems** of the **Boolean algebra** (the Boolean algebra will be studied in detail in the next chapter).
- Those theorems are called **De Morgan's theorems**:

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

- Where A and B are two **Boolean variables**
- (A Boolean variable is that which can **only take values 0 and 1**).

© Department of Physics, University of Babylon, 2019.

2.4.5 The exclusive-OR gate:

- The **exclusive-OR** gate **outputs a high level only**
- If the **inputs** are at **different logic levels**, either 0 and 1 or 1 and 0. Conversely, its **output is low**
- If the **inputs** are **at the same logic levels**. The **exclusive-OR gate** is sometimes called **XOR gate**.

- **Truth table:**

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

- Truth table:

- **Symbol:**




© Department of Physics, University of Babylon, 2019.

10

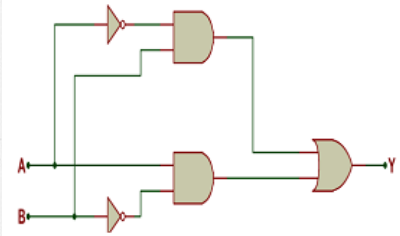Exercise 2.10:

- Let us consider following gate circuit:



- a. Determine the expression of the output.
 ➤ b. Deduce the truth table.
 ➤ c. Conclude.

➤ **Remark 2.5:**

- From the exercise above the following property can be deduced:

$$\overline{A}.\overline{B} + A.B = \overline{A \oplus B}$$